

Design Theory for High-Order Incremental Converters

János Márkus and Gábor C. Temes

markus@mit.bme.hu

Budapest University of Technology and Economics

Dept. of Measurement and Information Systems

and

Oregon State University

School of Electrical Engineering and Computer Science



OREGON STATE
UNIVERSITY

Powered by L^AT_EX 2_ε

Outline (Highlights)

- Digital measurement of DC signals
- Incremental (integrating) $\Delta\Sigma$ converter basics
- Analysis of higher-order architectures
- Digital filter design techniques

Digital Measurement of DC Signals

- **Applications**
 - **Sensors (seismic, pressure, temperature...)**
 - **Process monitoring and control**
 - **Instrumentation, digital voltmeter**

Digital Measurement of DC Signals

● Applications

- Sensors (seismic, pressure, temperature...)
- Process monitoring and control
- Instrumentation, digital voltmeter


● Requirements

- Low offset- and gain-error
- Good linearity, high accuracy (up to 18-20-24 bits)
- Low power consumption
- Low speed

A/D Converters for DC Measurement


- **Classical Nyquist-rate Converters**
 - **Dual-slope, V-to-freq converters**
 - **Sensitivity to noise and mismatches**
- **$\Delta\Sigma$ converters**
 - **Producing offset and tones**
 - **Non-multiplex**
- **Incremental converter**
 - + **Great tolerance**
 - + **No tones and offset**

First-Order Converter [robert84]

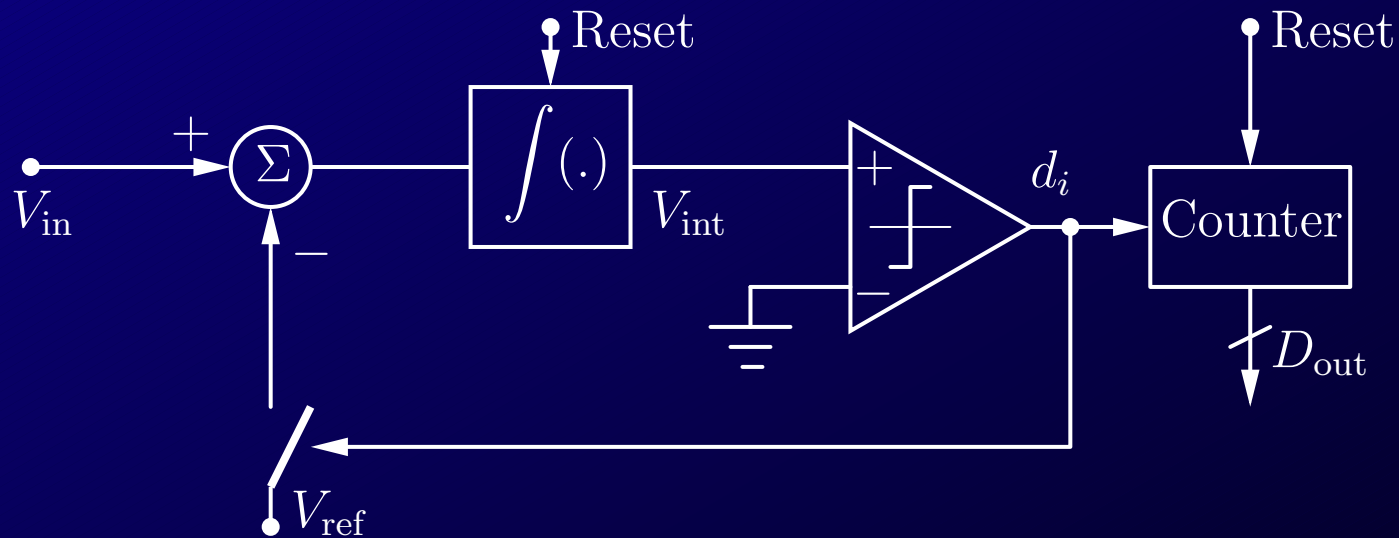

- Based on a $\Delta\Sigma$ structure
- Transient operation, simpler digital filter
- No-latency, one-shot, one-cycle, no-missing-code, charge-balancing $\Delta\Sigma$ converter


Higher-Order Incremental Converters

 

Due to the higher loop-gain

- + Faster operation can be achieved**
- Scaling coefficients b and c_i are required**

Operation Principle I.

 


First integrator's output:

$$V_{i_1}[1] = b(V_{in}[0] - d_0 V_{ref})$$

$$V_{i_1}[n] = b \sum_{k=0}^{n-1} (V_{in}[k] - d_k V_{ref})$$



Operation Principle II.

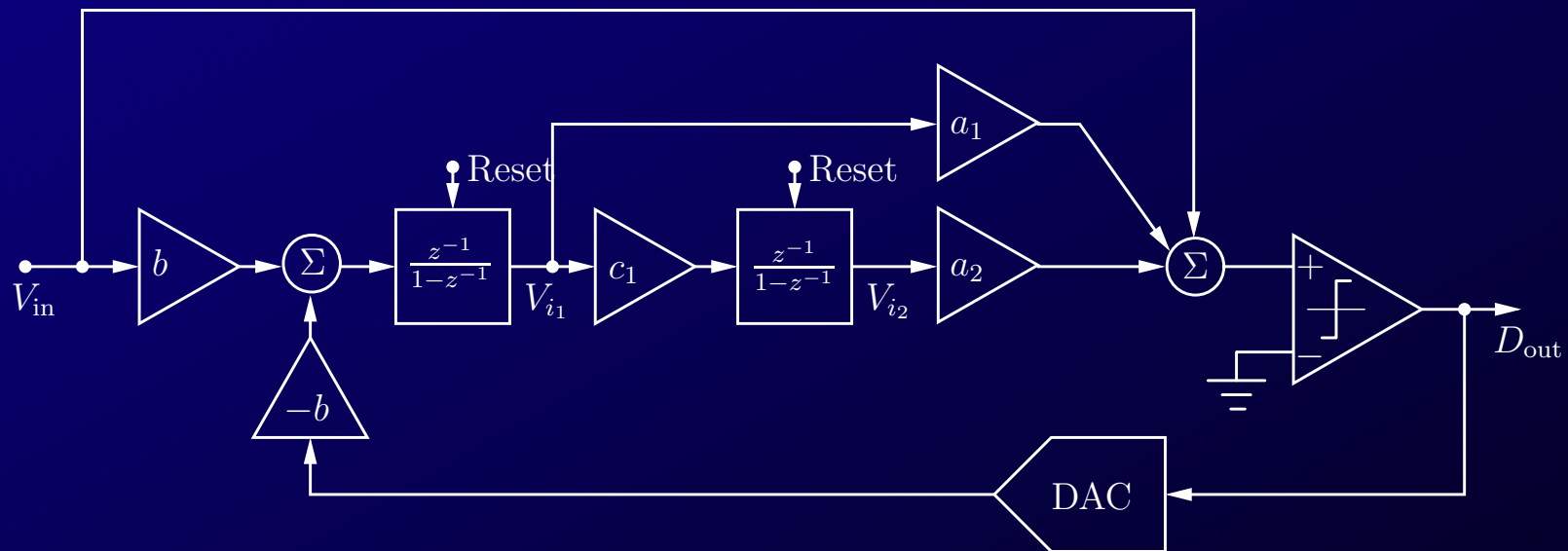

Second integrator's output:

$$V_{i_2}[n] = c_1 \sum_{l=0}^{n-1} V_{i_1}[l] = c_1 b \sum_{l=0}^{n-1} \sum_{k=0}^{l-1} (V_{in}[k] - d_k V_{ref})$$



Operation Principle III.

Second integrator's output:

$$V_{i_2}[n] = c_1 b \sum_{l=0}^{n-1} \sum_{k=0}^{l-1} (V_{\text{in}}[k] - d_k V_{\text{ref}})$$

If $V_{i_2}[n]$ is bounded by $\pm V_{\text{ref}}$ (i.e. stable), then (assuming DC input):

$$-\frac{2!}{(n-1)n} \frac{1}{c_1 b} V_{\text{ref}} < V_{\text{in}} - \frac{2!}{(n-1)n} V_{\text{ref}} \sum_{l=0}^{m-1} \sum_{k=0}^{l-1} d_k < \\ + \frac{2!}{(n-1)n} \frac{1}{c_1 b} V_{\text{ref}}$$

Output Calculation

$$\frac{\hat{V}_{\text{in}}}{V_{\text{ref}}} = \frac{2!}{(n-1)n} \sum_{l=0}^{m-1} \sum_{k=0}^{l-1} d_k$$

Properties:

- + **The output is independent of the scaling coefficients b and c_i**
- + **The quantization error is available in analog form**
($V_{i_2}[n] = -2V_{\text{ref}}e_q$)
- **Does not suppress periodic noise disturbances**

Resolution

The LSB value is

$$V_{\text{LSB}} = \frac{2 \cdot 2!}{(n-1)n c_1 b} V_{\text{ref}},$$

thus, the resolution becomes

$$n_{\text{bit}} = \log_2 \left(\frac{2V_{\text{ref}}}{V_{\text{LSB}}} \right) = \log_2 \left(c_1 b \frac{(n-1)n}{2!} \right) \\ \approx 2 \log_2(n) + \log_2(c_1 b) - 1$$

Properties:

$$+ n_{\text{bit}} \sim 2 \log_2(n)$$

– n_{bit} **depends on the scaling coefficients**

Effect of the Scaling Coefficients

- Resolution increases rapidly with n
- $b < 1$, $c_i < 1$, both are inversely proportional to n
- For 16-bit resolution $n = 363$ is required if $b = 1$,
 $c_i = 1$
- With proper scaling, this goes up ($n \geq 537$)
- One can find the lowest n easily by a couple of iterative simulations

Digital Filter Design I.


Recalling the output-calculation:

$$\frac{\hat{V}_{in}}{V_{ref}} = \frac{2!}{(n-1)n} \sum_{l=0}^{m-1} \sum_{k=0}^{l-1} d_k$$

- **Direct Realization: Cascade-of-Integrators (CoI) filter**
- **First-order integration cancels periodic disturbances if operation time matches $1/f_l$**
 - **Higher-order integration does not cancel periodic disturbances**

Digital Filter Design II.

Use CIC (sinc) filter instead of Col:

 

Properties:

- + L^{th} -order suppression of line frequency disturbances
- Requires more cycles to fulfill a given resolution requirement

Comparison

Order of Modulator	Type of Digital Filter	Resolution (Accuracy)	Total Number of Cycles
1	1 integrator (counter)	16	65536
2	2 integrators	16	537
2	third-order sinc	16	576



Conclusion


- Digital measurement of DC signals
- Incremental (integrating) $\Delta\Sigma$ converter basics
 - First-order converter
- Analysis of higher-order architectures
 - Structure
 - Operation
- Digital filter design techniques
 - Cascade-of-Integrators (CoI) filter
 - CIC (sinc) filters

Acknowledgement

This research has been supported by the following grants:

- NSF Center for the Design of Analog and Digital Integrated Circuits (CDADIC)
- NSF US–Hungary Grant, under contract No. UX026A
- Hungarian Fund for Scientific Research, under contract No. OTKA T 033 053

First-Order Converter II. [robert84]

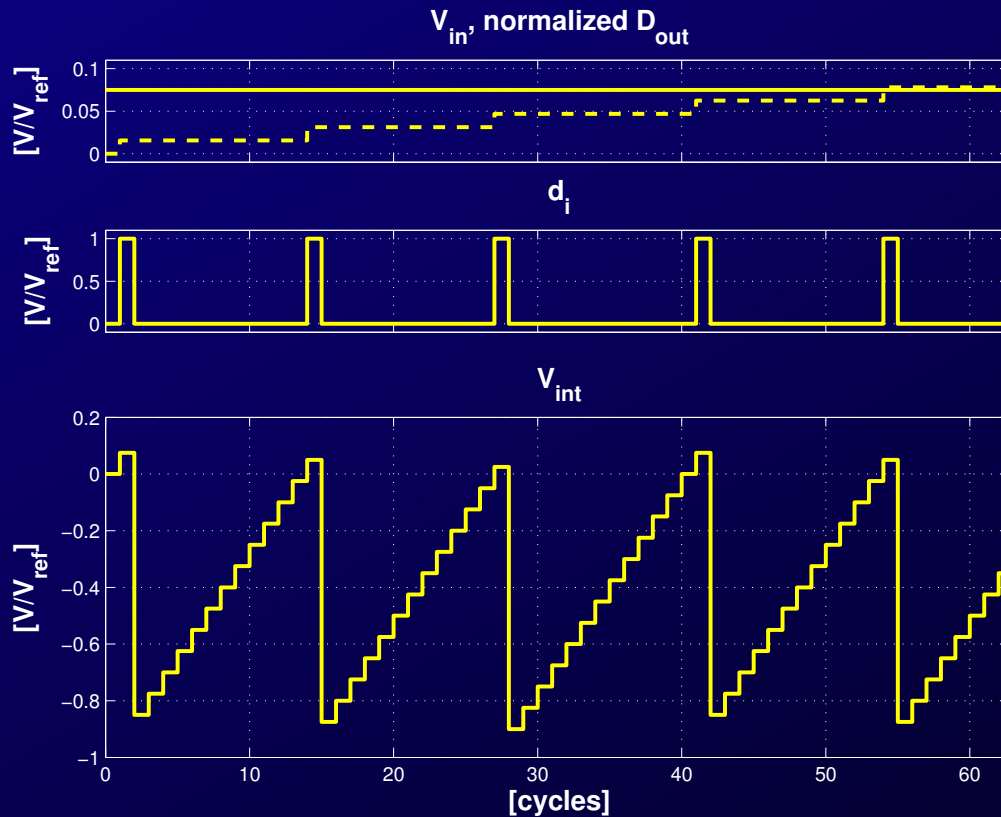

● $V_{in} = 0.075V_{ref}$


● $D_{out} = 5$

● $n_{bit} = 6$


● $n = 64$

● $D_{norm} =$
 $5/64 = 0.0781$

Improved Line Frequency Suppression

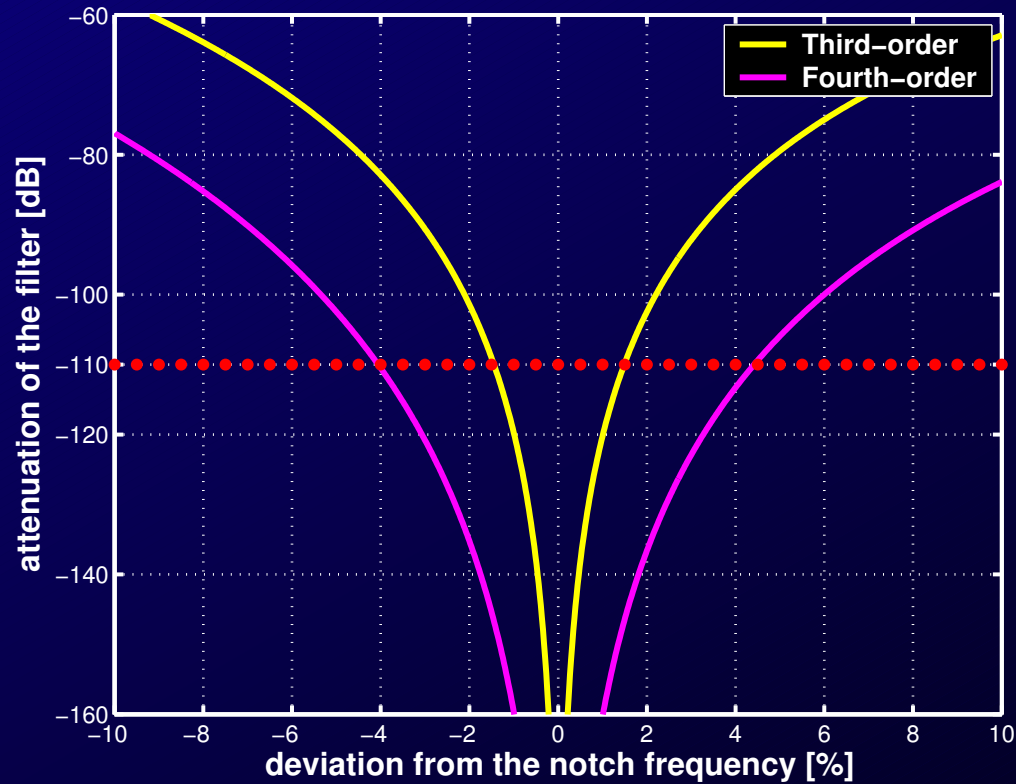

Improved Line Frequency Suppression

 

- Required if line and/or oscillator frequency drifts
- Can be realized by the rotated sinc-filter

